



# **D.A.V. PUBLIC SCHOOL, CRRC, Medical Road, Gaya**

**Sunday Test (Date – 03.12.2023)**

**Class – VI**  
**Sub. – Science**

**Time: 40 Min**  
**F.M. - 20**

## **SECTION – A (2X5=10)**

- Q1. Write the meaning of term 'electric circuit'?
- Q2. State the function of metallic strips used in a torch?
- Q3. Define conductor.
- Q4. Write the full form of
  - a) CFL
  - b) LED
- Q5. Name the three essential components of electric circuit.

## **SECTION – B (5X2=10)**

- Q1. Draw a well labeled diagram of a dry cell.
- Q2. Draw an electric circuit diagram using electric symbols of bulb, cell, connecting wires and electric switch.

**\*\*\***